TB6634FNG Usage considerations

Rev. 1.0

SummaryThe TB6634FNG is a controller IC for three-phase brushless DC motor. It controls the motor rotation speed by sine-wave current drive. It is developed for fan of home appliance.

TOSHIBA

Contents

Contents	2
1. Power supply	3
2. Notes in operating IC	3
3. Application circuit example	3
IC Usage Considerations	9
RESTRICTIONS ON PRODUCT USE	10

1. Power supply

Operating range of the power supply voltage is 6V to 16.5V. The absolute maximum rating of the power supply voltage is 18V that must not be exceeded, even for a moment. Do not exceed any of these ratings. Please use the IC within the range of the power dissipation.

2. Notes in operating IC

When the motor operation is turned off or configured low-speed rotation from normal speed rotation, the power supply may boost because the current is regenerated to the motor power supply by the influence of the back-electromotive force. Pay attention to change the motor rotation speed from high to low or off. Confirm and control the IC operation by experiments in decreasing the motor rotation speed slowly to avoid the destruction of the power device by power supply voltage boosting.

3. Application circuit example

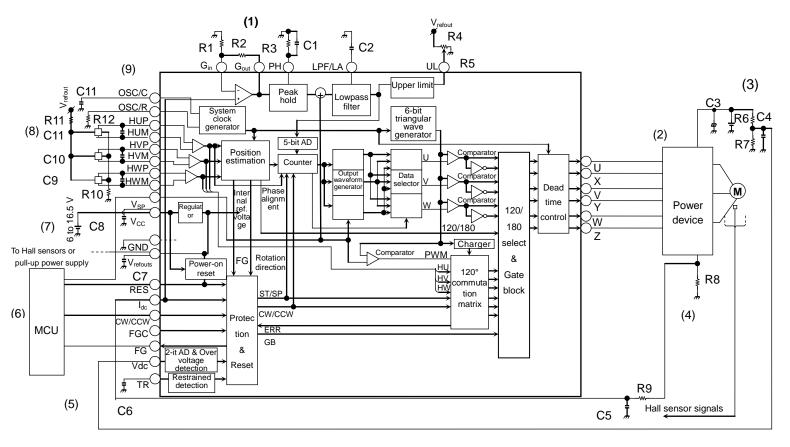


Figure 1 Application circuit example

(1) Setting lead angle

- Determine the lead angle by using the actual equipment because the lead angle level changes depending on the motor.
 - I . Drive the motor by necessary rotation number, short-circuit the UL terminal to the Vrefout terminal, apply the voltage (0 to 5 V) externally to the LPF/LA terminal, and confirm the current waveform or efficiency to determine the most appropriate voltage of the LPF/LA terminal.
 - II. Amplify the voltage conversion value of the shunt resistance by external resistances of Gin and Gout terminals to set the voltage of the LPF/LA terminal determined in 'step I'.
 - III. Drive the motor and confirm that the voltage of the LPF/LA terminal equals the value that is determined in 'step I'.
- 2. Recommended setting value
 - •PH terminal: R3=100 kΩ/C1=0.1 μF
 - LPF/LA terminal: C2=0.1 µF
 - •Gin terminal/Gout terminal (gain=(1+(R2/R1)) When R1=10 k Ω /R2=100 k Ω , 11 times
- 3. Setting fixed lead angle
 - I . Pattern A
 - •Gin terminal/Gout terminal: R1=OPEN/R2=short-circuit
 - •PH terminal: OPEN
 - •LPF/LA terminal: short-circuit to Vrefout terminal
 - UL terminal: input fixed voltage
 - II. Pattern B

(Voltage changes unless the input impedance of the fixed voltage is not configured lower because the LPF/LA terminal is input/output terminal.)

- •Gin/Gout terminal: R1=OPEN/R2=short-circuit
- •PH terminal: OPEN
- ·LPF/LA terminal: input fixed voltage
- •UL terminal: short-circuit to Vrefout terminal


- 4. Reference data of lead angle setting I . Reference data of lead angle setting

 - Measuring method

Result of confirming the lead angle (steps) in the test mode by changing UL applied voltage.

Conditions

VSP and LA/LPF=6V

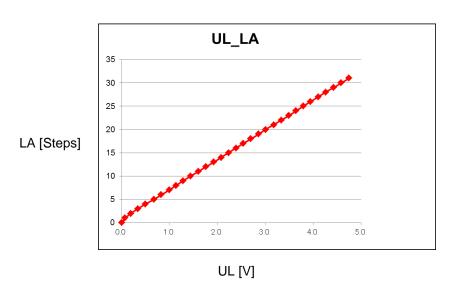

LA (steps)	UL[V]
0	0.00
1	0.07
2	0.19
3	0.34
4	0.49
5	0.67
6	0.82
7	0.99
8	1.14
9	1.28
10	1.44
11	1.60
12	1.76
13	1.92
14	2.07
15	2.23
16	2.39
17	2.54
18	2.69
19	2.86
20	3.00
21	3.17
22	3.33
23	3.49
24	3.64
25	3.79
26	3.94
27	4.11
28	4.26
29	4.42
30	4.58
31	4.74


II. Reference data of lead angle setting


Measuring method


Result of confirming the lead angle (steps) in the test mode by changing VSP and applied voltage of ldc in each gain configuration.

Conditions

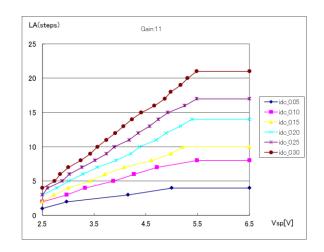 $PH=100k\Omega/0.1\mu F$ $LPF/LA=0.1\mu F$



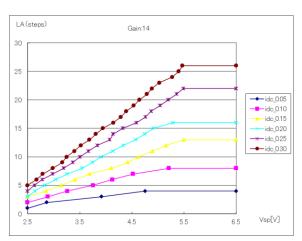

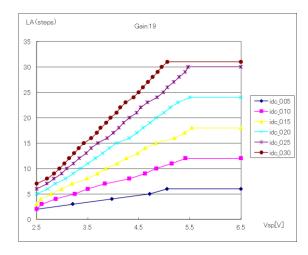

(2) Power device

Connect the capacitor to reduce the noise and variation of the voltage of the motor power supply. Wiring pattern should be taken wide because large current flows in the power supply, ground, and outputs of the power device. Specially, for the ground, wiring pattern should be taken as wide as possible.

Recommended device

TPD4123AK (500 V/1 A)

TPD4144AK (500 V/2 A)

TPD4135AK (500 V/3 A)

(3) Vdc terminal setting

The voltage of Vdc terminal is configured by the resistive divider of R6 and R7.

In case variation of the voltage of Vdc terminal and the noise are large, connect the capacitor to C4.

The accuracy of the resistance is recommended to be set 1% or less.

(4) Idc terminal setting

Idc terminal inputs the functions of current limit and lead angle by detecting the output current with the shunt resistance of R8.

The current limit function works when the voltage of Idc terminal rises 0.3V (typ.) or more.

Current limit value=0.3V/R8

Ex.) When R8= 0.2Ω ,

Current limit value=0.3V/0.2Ω=1.5A

Lead angle function should be set by referring to the lead angle configuration shown in (1) above.

Though the system of current limit incorporates the low pass filter ($200k\Omega$, 5pF) and the digital filter (5clk@fosc), the filter should be connected to C5 and R9 corresponding to the noise of the power block Time constant of C5 / R9 is recommended to 2µs or less.

(5) TR terminal setting

Motor lock detection operates repeatedly (operating time: stopping time=1:6). This term can be set by the external capacitor (C6) of TR terminal.

- Driving term Ton[s]=C6x(VH—VL)x2/lx500 counters
- Stopping term Toff[s]=C6x(VH—VL)x2/lx3000 counters

```
•Example: When C6 = 0.01μF,
I = 3.15uA (typ.), VH= 2 V (typ.), VL= 0.5V (typ.),
Ton[s] =4.76s (typ.) and Toff[s] =28.57s (typ.).
```

•In case motor lock detection is not used, connect TR terminal to GND.

(6) RES terminal

When input signal (RES) level is low, commutation signal outputs low. When RES is high, it is released with every carrier frequency and re-starts.

When RES is low, the boosting strap capacitor is not charged (refresh).

To charge the boosting strap capacitor in recovering mode, input the voltage command as follows; 1.0 V < Vsp \le 2.1 V

(7) VCC terminal/Vrefout terminal and GND terminal setting

Connect the capacitor between VCC and GND, and Vrefout and GND as close to the IC as possible. Specifically connect the electrolytic capacitor and ceramic capacitor in parallel between VCC and GND to reduce the noise and the variation of voltage.

Take the wiring pattern of the GND terminal of the IC widely not to be influenced by the GND of motor power system.

Vrefout terminal is used for the reference power supply of internal IC. Do not forget to connect the capacitor regardless of using Vrefout power supply.

VCC-GND: C8:

Electrolytic capacitor 1μF to 47μF Ceramic capacitor 0.001μF to 1μF Vrefout-GND Ceramic capacitor 0.001μF to 1μF

(8) Hall signal setting

Hall signal input terminal may cause malfunction of the IC because it has a high impedance and easy to be influenced by noise. To avoid the malfunction, connect the capacitors of C9 between HUP and HUM, C10 between HVP and HVM, and C11 between HWP and HWM terminals. The recommended capacitor range is 0.001µF to 0.1µF.

Input voltage range of the same phase of the hall signal is 1.5V to 3.5V. So, adjust the resistors of R10 and R11 to set the voltage of the input signal within this range.

(9) OSC/C terminal and OSC/R terminal setting

Formula of the frequency configured by OSC/R: R and OSC/C: C is as follows;

- Oscillation frequency fosc=4.485/(0.29CR) [Hz]
- Carrier frequency Fc=4.485/(252×0.29CR) [Hz]
- •Example 1: When OSC/R: 9.1kΩ and OSC/C: 330pF, Carrier frequency Fc (20) =20.5 kHz
- Example 2: When OSC/R: 10kΩ and OSC/C: 330pF,
 Carrier frequency Fc (18) =18.5 kHz

OSC/R: R and OSC/C: C should be connected as close to the IC as possible in order not to be influenced by noise and wiring impedance. Use the resistor and capacitor whose accuracy is 1% or less.

IC Usage Considerations

Notes on handling of ICs

- [1] The absolute maximum ratings of a semiconductor device are a set of ratings that must not be exceeded, even for a moment. Do not exceed any of these ratings.
 - Exceeding the rating(s) may cause the device breakdown, damage or deterioration, and may result injury by explosion or combustion.
- [2] Use an appropriate power supply fuse to ensure that a large current does not continuously flow in case of over current and/or IC failure. The IC will fully break down when used under conditions that exceed its absolute maximum ratings, when the wiring is routed improperly or when an abnormal pulse noise occurs from the wiring or load, causing a large current to continuously flow and the breakdown can lead smoke or ignition. To minimize the effects of the flow of a large current in case of breakdown, appropriate settings, such as fuse capacity, fusing time and insertion circuit location, are required.

Points to remember on handling of ICs

- (1) Over current Protection Circuit
 - Over current protection circuits (referred to as current limiter circuits) do not necessarily protect ICs under all circumstances. If the over current protection circuits operate against the over current, clear the over current status immediately.
 - Depending on the method of use and usage conditions, such as exceeding absolute maximum ratings can cause the over current protection circuit to not operate properly or IC breakdown before operation. In addition, depending on the method of use and usage conditions, if over current continues to flow for a long time after operation, the IC may generate heat resulting in breakdown.
- (2) Thermal Shutdown Circuit
 - Thermal shutdown circuits do not necessarily protect ICs under all circumstances. If the thermal shutdown circuits operate against the over temperature, clear the heat generation status immediately depending on the method of use and usage conditions, such as exceeding absolute maximum ratings can cause the thermal shutdown circuit to not operate properly or IC breakdown before operation.

9 / 10 2016-05-25

RESTRICTIONS ON PRODUCT USE

- Toshiba Corporation, and its subsidiaries and affiliates (collectively "TOSHIBA"), reserve the right to make changes to the information in this document, and related hardware, software and systems (collectively "Product") without notice.
- This document and any information herein may not be reproduced without prior written permission from TOSHIBA. Even with TOSHIBA's written permission, reproduction is permissible only if reproduction is without alteration/omission.
- Though TOSHIBA works continually to improve Product's quality and reliability, Product can malfunction or fail. Customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of Product could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Before customers use the Product, create designs including the Product, or incorporate the Product into their own applications, customers must also refer to and comply with (a) the latest versions of all relevant TOSHIBA information, including without limitation, this document, the specifications, the data sheets and application notes for Product and the precautions and conditions set forth in the "TOSHIBA Semiconductor Reliability Handbook" and (b) the instructions for the application with which the Product will be used with or for. Customers are solely responsible for all aspects of their own product design or applications, including but not limited to (a) determining the appropriateness of the use of this Product in such design or applications; (b) evaluating and determining the applicability of any information contained in this document, or in charts, diagrams, programs, algorithms, sample application circuits, or any other referenced documents; and (c) validating all operating parameters for such designs and applications. TOSHIBA ASSUMES NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.
- PRODUCT IS NEITHER INTENDED NOR WARRANTED FOR USE IN EQUIPMENTS OR SYSTEMS THAT REQUIRE EXTRAORDINARILY
 HIGH LEVELS OF QUALITY AND/OR RELIABILITY, AND/OR A MALFUNCTION OR FAILURE OF WHICH MAY CAUSE LOSS OF
 HUMAN LIFE, BODILY INJURY, SERIOUS PROPERTY DAMAGE AND/OR SERIOUS PUBLIC IMPACT ("UNINTENDED USE"). Except for
 specific applications as expressly stated in this document, Unintended Use includes, without limitation, equipment used in nuclear facilities,
 equipment used in the aerospace industry, medical equipment, equipment used for automobiles, trains, ships and other transportation, traffic
 signaling equipment, equipment used to control combustions or explosions, safety devices, elevators and escalators, devices related to
 electric power, and equipment used in finance-related fields. IF YOU USE PRODUCT FOR UNINTENDED USE, TOSHIBA ASSUMES NO
 LIABILITY FOR PRODUCT. For details, please contact your TOSHIBA sales representative.
- · Do not disassemble, analyze, reverse-engineer, alter, modify, translate or copy Product, whether in whole or in part.
- Product shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.
- The information contained herein is presented only as guidance for Product use. No responsibility is assumed by TOSHIBA for any infringement of patents or any other intellectual property rights of third parties that may result from the use of Product. No license to any intellectual property right is granted by this document, whether express or implied, by estoppel or otherwise.
- ABSENT A WRITTEN SIGNED AGREEMENT, EXCEPT AS PROVIDED IN THE RELEVANT TERMS AND CONDITIONS OF SALE FOR
 PRODUCT, AND TO THE MAXIMUM EXTENT ALLOWABLE BY LAW, TOSHIBA (1) ASSUMES NO LIABILITY WHATSOEVER,
 INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING
 WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (2)
 DISCLAIMS ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO SALE, USE OF PRODUCT, OR
 INFORMATION, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE,
 ACCURACY OF INFORMATION, OR NONINFRINGEMENT.
- Do not use or otherwise make available Product or related software or technology for any military purposes, including without limitation, for the
 design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass
 destruction weapons). Product and related software and technology may be controlled under the applicable export laws and regulations
 including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export
 and re-export of Product or related software or technology are strictly prohibited except in compliance with all applicable export laws and
 regulations.
- Please contact your TOSHIBA sales representative for details as to environmental matters such as the RoHS compatibility of Product. Please
 use Product in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without
 limitation, the EU RoHS Directive. TOSHIBA ASSUMES NO LIABILITY FOR DAMAGES OR LOSSES OCCURRING AS A RESULT OF
 NONCOMPLIANCE WITH APPLICABLE LAWS AND REGULATIONS.

10 / 10 2016-05-25